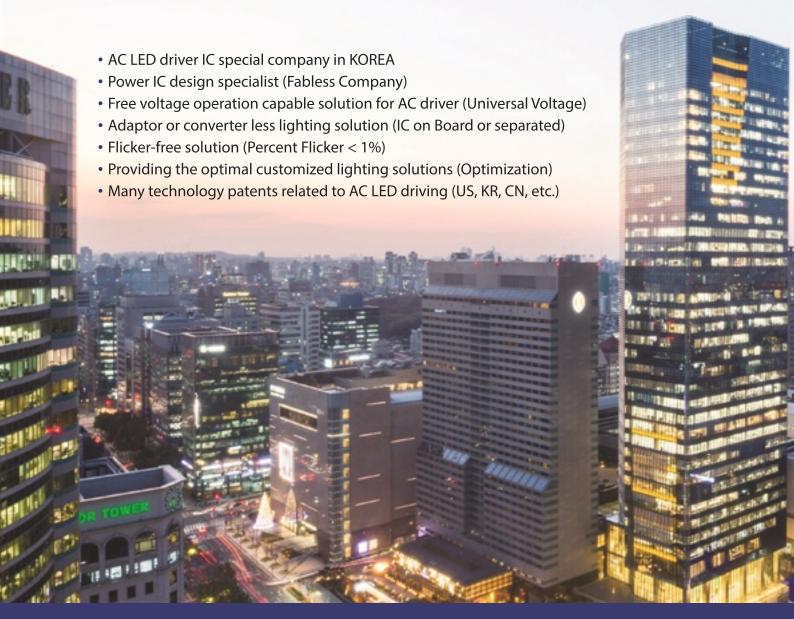


### POINT TEK

# Power Integration Technology of Korea



### **About us**

• Company Fabless company specializing in LED lighting

• **Specialty** Core competence in power IC and power electronics

History Established July 2009
 (Located in Yongin-City, Gyeonggi-Do, Korea)

• Business
Model

LED driver IC & LED lighting module sales

#### History



AC direct LED driver IC & AC direct driver IC integrated lighting module Product

◆ Linear type flicker-free AC direct LED driver IC

Linear type simultaneous driving AC direct LED driver IC

1 Linear type dual voltage driving AC direct LED driver IC

Linear type universal voltage driving AC direct LED driver IC


 Production 100KK (EA/Month) IC Based 100K (EA/Month) Down light module based Capacity

## Synchronous AC LED Driver IC

Parameters	M Company	R Company	Point Tek
Efficiency (%)	> 80	> 80	> 80
Power Factor	> 0.99	> 0.99	0.998
THD (%)	< 9	< 9	8.06
Maximum Output Power under 120V/AC (W)	20	12 <	35
Number of Turn-on LED strings at period (1) (EA)	1	1	4
Number of Turn-on LED strings at period (2) (EA)	2	2	4
Number of Turn-on LED strings at period (3) (EA)	3	3	4
Number of Turn-on LED strings at period (4) (EA)	4	4	4
LED Utilization in four-string LED (%)	62.5	62.5	100

PT's driver turns on LEDs synchronously for all voltage ranges but others turn on sequentially No other company provide 100% LED utilization in AC LED driver

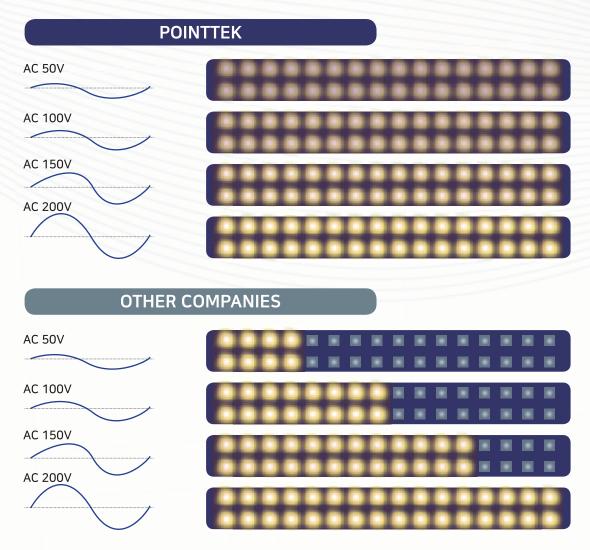▶ World First Synchronous AC LED Driving Technology (PT's Patented)



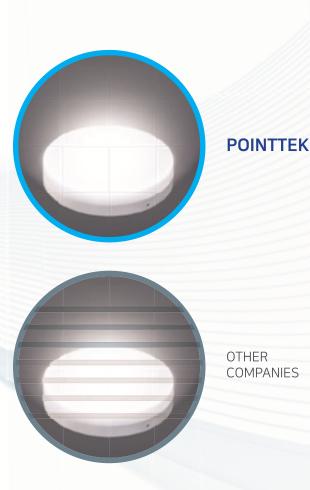
### Flicker-Free **AC LED Driver IC**

- ▶ No LED Blinking
- ▶ Percent Flicker: less than 1 %
- ▶ Dimmable Solutions (Triac, 0 to 10, etc.)
- ► Meet all new Flicker standards (PST, SVM, CA-Title 24, etc.)
- ► Smaller capacitance than before
- ▶ World best solution for Flicker-free AC LED Driver IC (PT's Patent)







### Universal AC LED Driver IC

Automatically adjusted Series-Parallel connections depending on the input voltage Automatically adjusted the LED current according to the input voltage PT's patented universal solution provides the same power over wide voltage ranges.



120V / 10.7W




220V / 9.8W




277V / 10.2W

#### **POINTTEK**

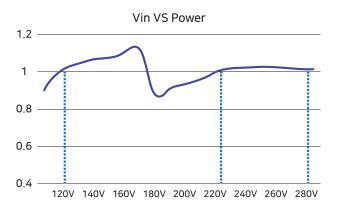

#### **OTHER COMPANIES**

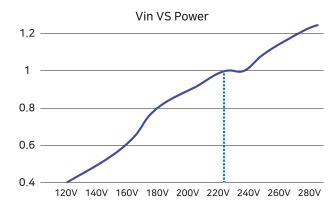


### **Product List**

Device ID	LED Channel & Characteristics	Recommended Applications
PT5010X	- 4 Channel - Low Voltage (for dispersion of heat)	- Lamps - Down Light * Middle - High power
PT7120X	- 2-4 Channel - Low Voltage - Universal Voltage	- High Bay, Flood Light - Explosion Proof Light * Middle - High power
PT1011X	- 2 Channel - High Voltage (for dispersion of heat)	- Low Cost Lamps & Bulb - Down Light - Tube * Low power
PT1010X (A)	- 3 Channel - High Voltage (for dispersion of heat)	- Low Cost Lamps - Down Light - Tube * Low power
PT1050X	- 5 Channel - Universal Voltage - Middle or High Power	- Troffer - High Bay, Flood Light - Explosion Proof Light * Middle - High power
PT7111X	- Flicker-free - Only 1 Capacitor	- Indoor Lighting - Special Lighting * Low power
PT8410X	- Sub IC for dimming - Flicker-free	- Indoor Lighting - Special Lighting * Low power
PT1020X	- Mirror IC (Sub IC) - For Synchronous driving	- LED Fluorescent Lamp - Troffer

6x6 QFN

# **Driver IC PKG** Type List

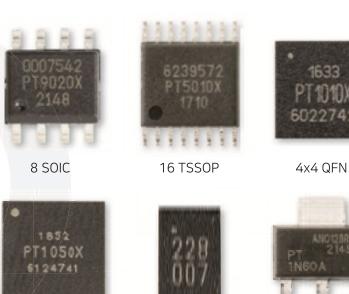

2x3 DFN

SOT-223

# **Downlight Series**



Volt	Watt	Lm	ССТ	CRI	%Flicker	PF
120	15	1000↑	3000	90	20	0.96

#### 6 inch model

(PT1010X / PT1520X Adopted)

- ► LED Driver integrated(by IC)
- ► Switching dimmable
- ▶ Dimming (0 to 10, triac)
- ► Satisfy CA Title 24
- ▶ %Flicker < 30%



Volt	Watt	Lm	ССТ	CRI	%Flicker	PF
120	7	490↑	3000	90	0.2	0.98

#### 4 inch model

(PT7111X Adopted)

- ► LED Driver integrated(by IC)
- ► Analog dimmable (0 to 10)
- ▶ Satisfy CA Title 24
- ▶ %Flicker < 1%
- ► Small Capacitor

# Parking lot Series



- ▶ Dimming (0 to 10, triac)

► LED Driver integrated(by IC)

- ▶ Satisfy CA Title 24
- ▶ %Flicker < 30%
- ▶ Wide voltage range (AC 120V,220V~240V,277V)

Volt	Watt	Lm	ССТ	CRI	%Flicker	PF
120	10.7	1000↑	3000	90	26	0.92
220	10.4	1000↑	3000	90	18	0.99
277	10.8	1000↑	3000	90	14	0.99

#### 2ft model

(PT7111X Adopted)

- ► LED Driver integrated(by IC)
- ► Analog dimmable (0 to 10)
- ▶ Satisfy CA Title 24
- ▶ %Flicker < 1%
- ▶ Small Capacitor

Volt	Watt	Lm	ССТ	CRI	%Flicker	PF
120	20	1600↑	3000	90	0.2	0.98

# High-bay Series





Volt	Watt	Lm	ССТ	CRI	%Flicker	PF
220	150	17,250	5700	80	100	0.99

#### 150W model

(PT1050X Adopted)

- ► LED Driver integrated(by IC)
- ▶ High efficiency



# Volt Watt Lm CCT CRI %Flicker PF 220 200 23,000 5700 80 100 0.99


#### 200W model

(PT1050X Adopted)

- ► LED Driver integrated(by IC)
- ► High efficiency
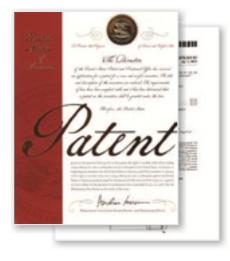
### **Patents**

Many patents for AC Direct driving technologies such as flicker-free driving technology, universal driving technology, and EMI-reduced driving technology.







**USA KOREA CHINA** 

### Awards & Certificates

ISO 9001:2015

Certificate of Industrial R&D Center Certificate of Promising Small And Medium-Sized Enterprise Awarded "Excellent company in new technology development" for LED part Awarded "2019 Korea Patent Excellence Award in Electric and Electronic"



ISO 9001:2015



Certificate of Industrial **R&D** Center



Certificate of **Promising Small** And Medium-Sized Enterprise



Award for Excellent company in new technology development for LED part



2019 Korea Patent Excellence Award in Electric and Electronic





#326, 2nd Eng. Building, Dankook University, 152, Jukjeon-ro, Suji-gu, Yongin-si, Gyeonggi-do, Republic of Korea

info@point-tek.com

www.point-tek.com

